


# ECN 101

**Introduction to Electronics and Communication Engineering**



# Review

Integration crucial for modern technological development.




## Diode circuits

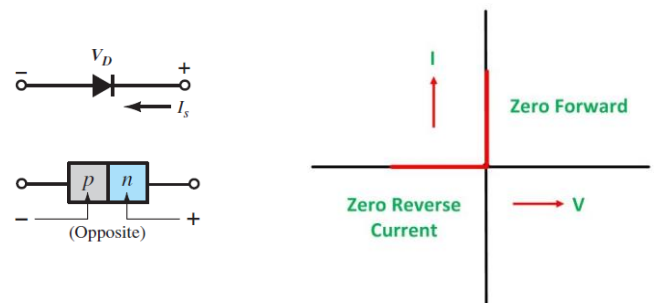

## Half wave rectifier

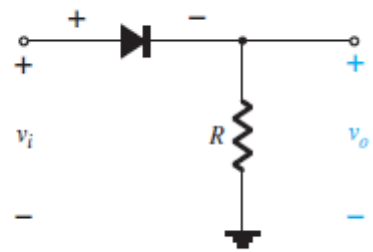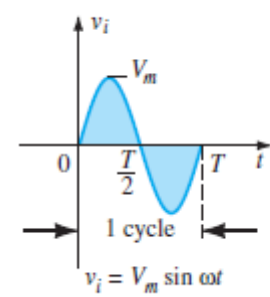


## Full wave rectifier

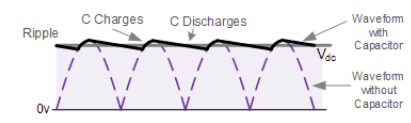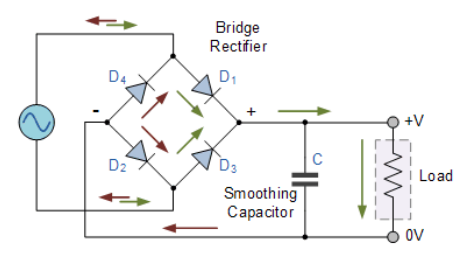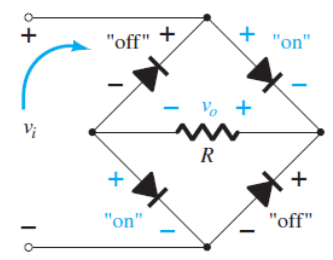

## Diode as clipper and clamper




## Diode as voltage regulator

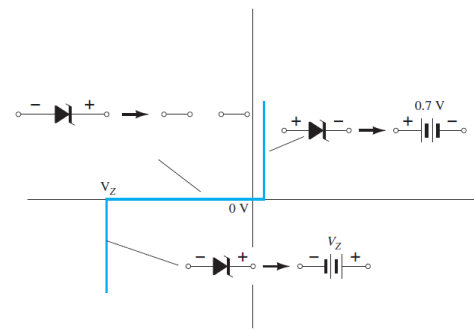


## Op-Amp basics
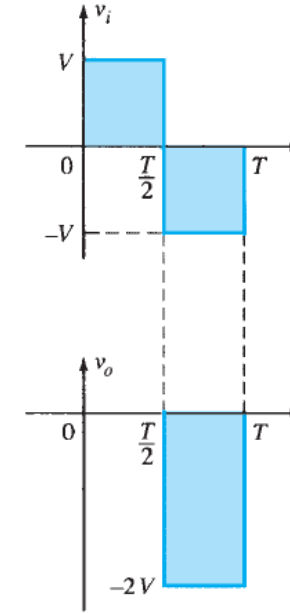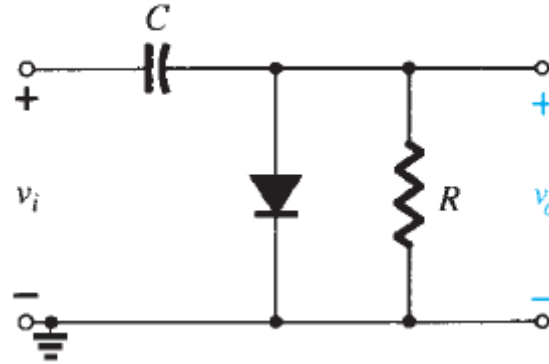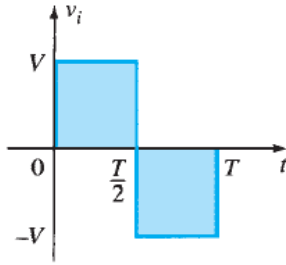
# Diode as clamper


Clamper is a circuit that changes the dc level of a waveform without changing its appearance.



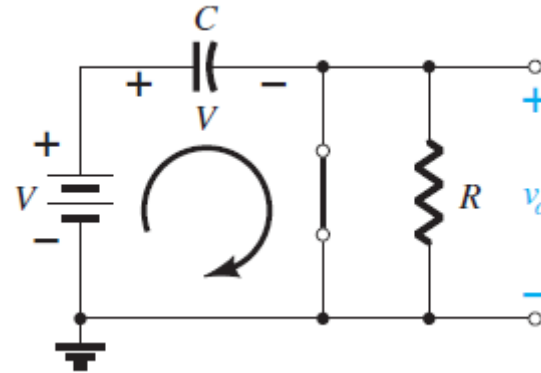During the period that the diode is in the 'on' state, assume that the capacitor will charge up instantaneously to a voltage level determined by the surrounding network.





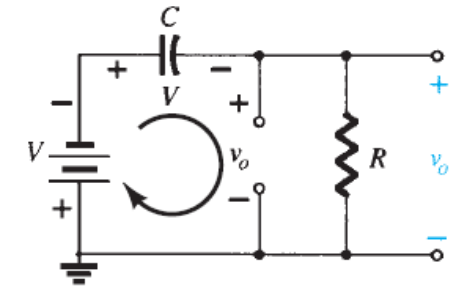Assume that during the period when the diode is in the 'off' state the capacitor holds on to its established voltage level.



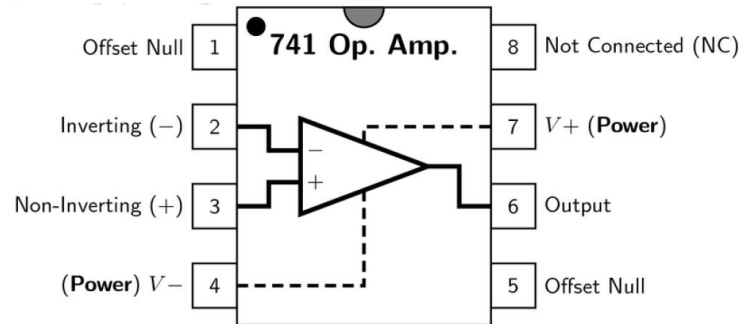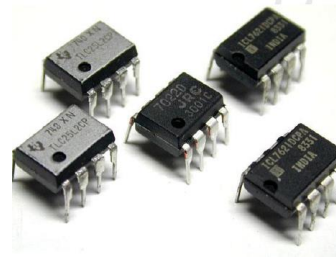
# Op-Amp: LM 741


- One of the most commonly used Op-Amp.
- Packaged device look like:



SCHEMATIC DIAGRAM

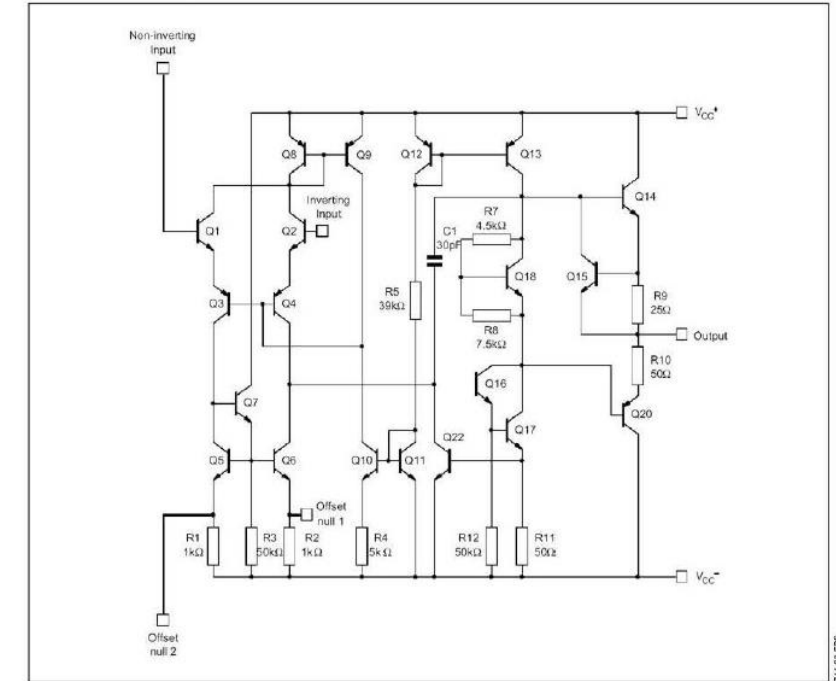


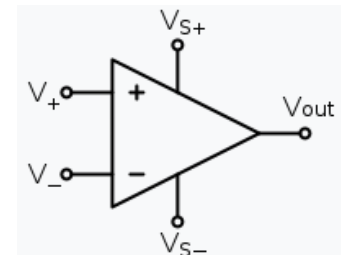- An Op-Amp contains several transistors, resistors, and a few capacitors and diodes.
- More simply, an Op-Amp is depicted as:


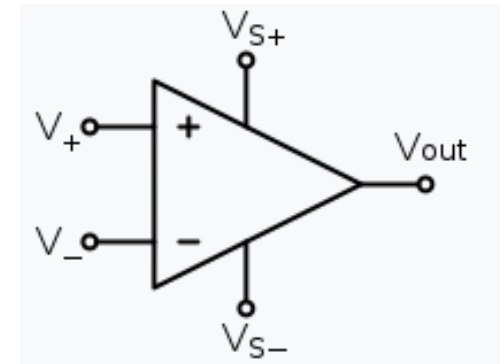
# Op-Amp in a nutshell


- The internal circuitry in the op-amp tries to force the voltage at the inverting input to be equal to the non-inverting input.
- While analyzing an Op-Amp circuit
  - Assume no current flows into either input terminal
  - Assume no current flows out of the output terminal





The output voltage is limited by the supply voltage.

## Op-Amp contd..

- Op-Amp is represented as:


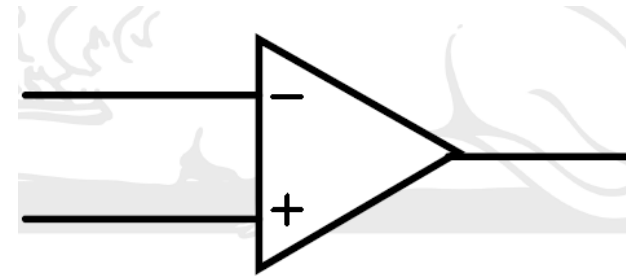


### Op-Amp functional model

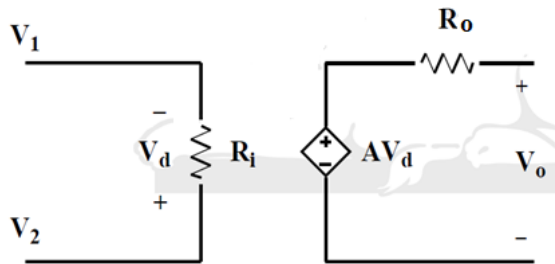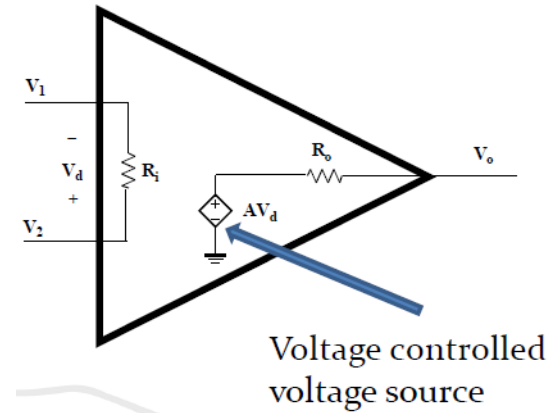




$$V_d = V_2 - V_1$$

**A** is the open loop gain.

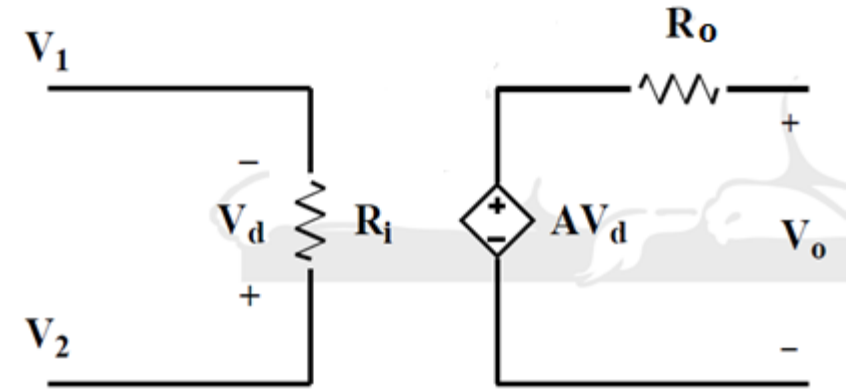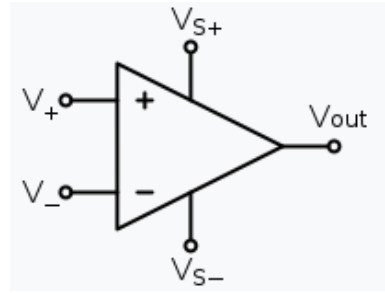

Parameter	Variable	Ideal Values	Typical Ranges
Open-Loop Voltage Gain	$A$	$\infty$	$10^5$ to $10^8$
Input Resistance	$R_i$	$\infty \Omega$	$10^5$ to $10^{13} \Omega$
Output Resistance	$R_o$	$0 \Omega$	$10$ to $100 \Omega$
Supply Voltage	$V_{cc}/V^+$ $-V_{cc}/V^-$	N/A N/A	$5$ to $30 V$ $-30V$ to $0V$

# Voltage transfer characteristics

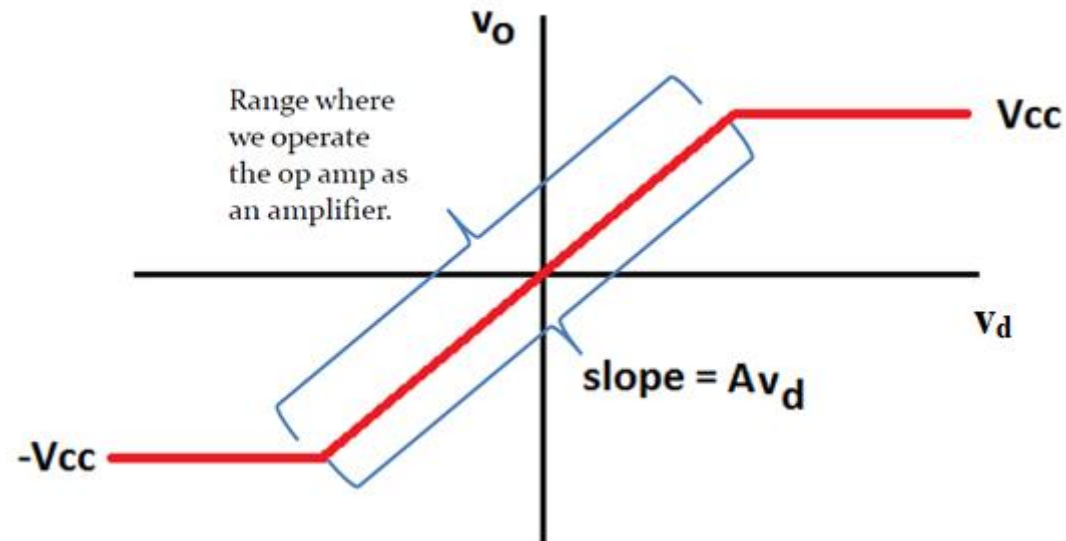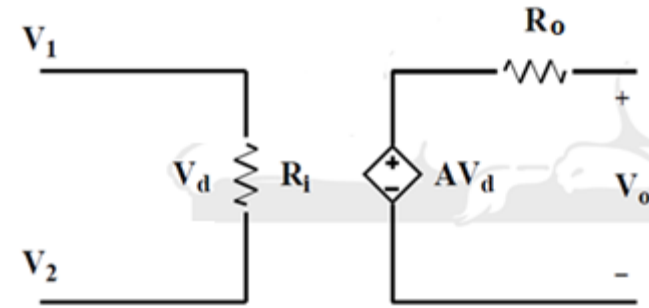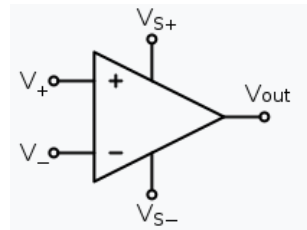




# Op-Amp analysis

$$R_i = \infty \Omega$$

– Therefore,  $i_1 = i_2 = 0A$


$$R_o = 0 \Omega$$

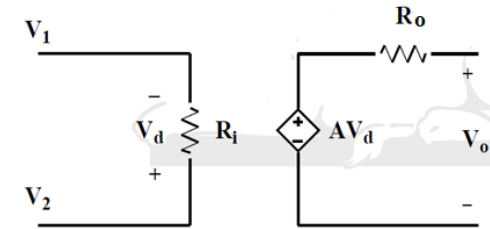

Rarely is the op amp limited to  $-V_{cc} < V_o < +V_{cc}$


$$V_d = 0V \text{ and so } V_1 = V_2$$

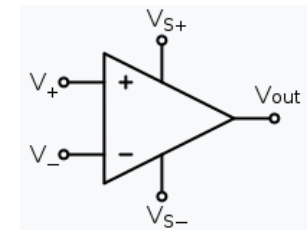- The internal circuitry in the op-amp tries to force the voltage at the inverting input to be equal to the non-inverting input.
- While analyzing an Op-Amp circuit
  - Assume no current flows into either input terminal
  - Assume no current flows out of the output terminal



# Op-Amp usages


## Inverting Amplifier

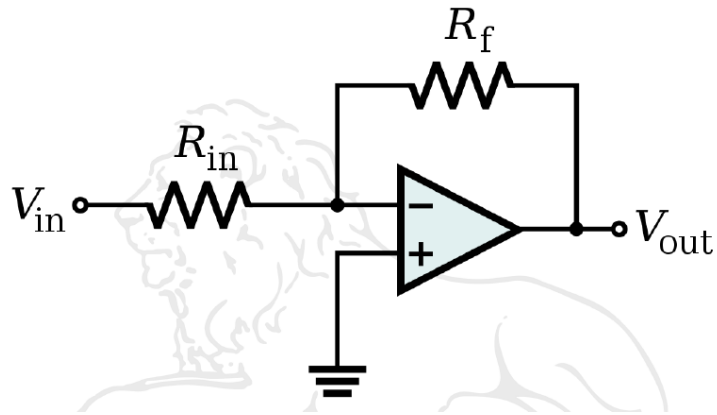

$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$

# Op-Amp usages


## Non-inverting Amplifier

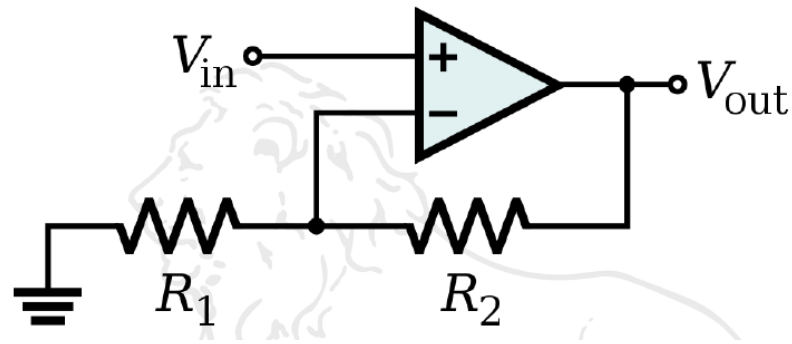

$$V_{out} = V_{in} \left( 1 + \frac{R_2}{R_1} \right)$$

# Op-Amp usages


## Differentiator

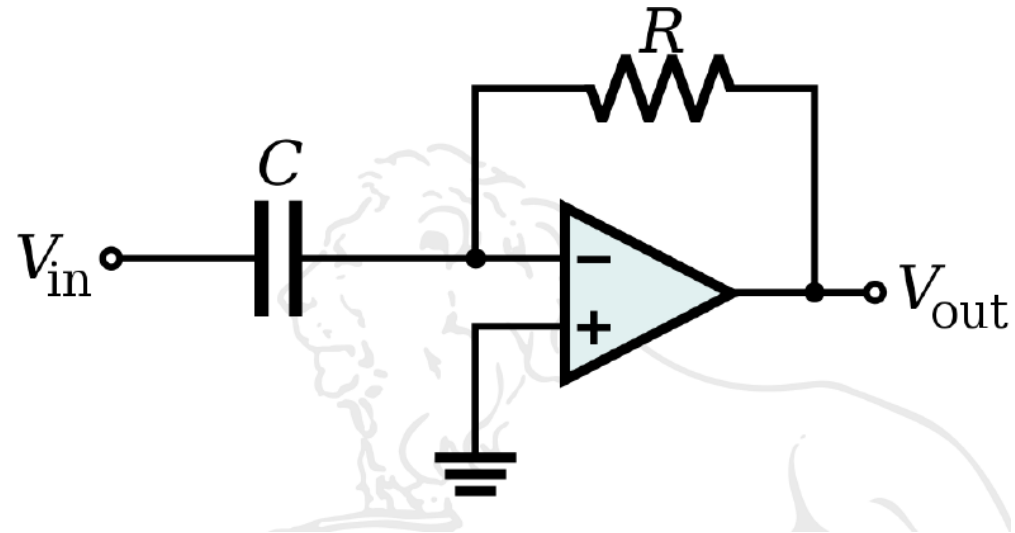

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

# Op-Amp usages


## Integrator

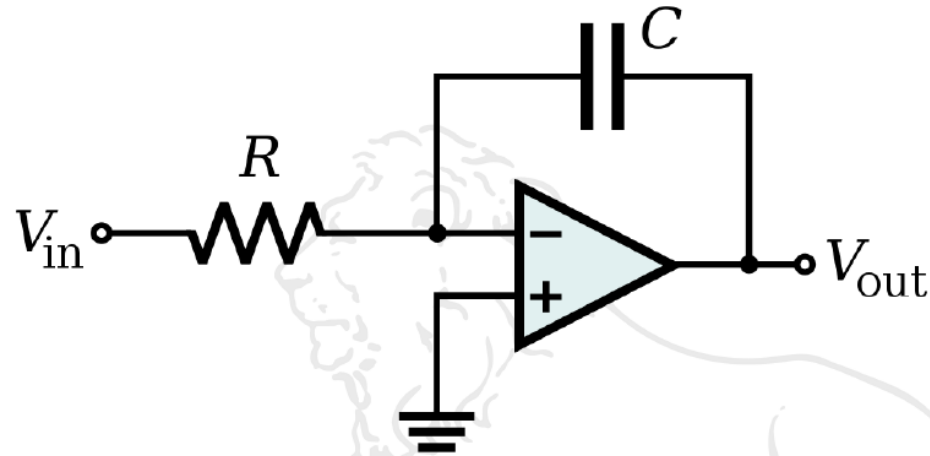

$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$

# Op-Amp usages


## Summing amplifier

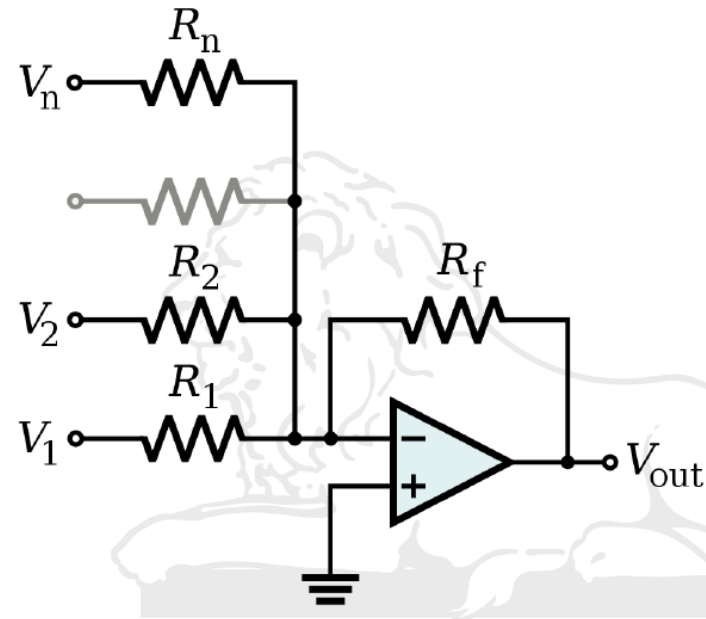

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

# Op-Amp usages

## Difference amplifier


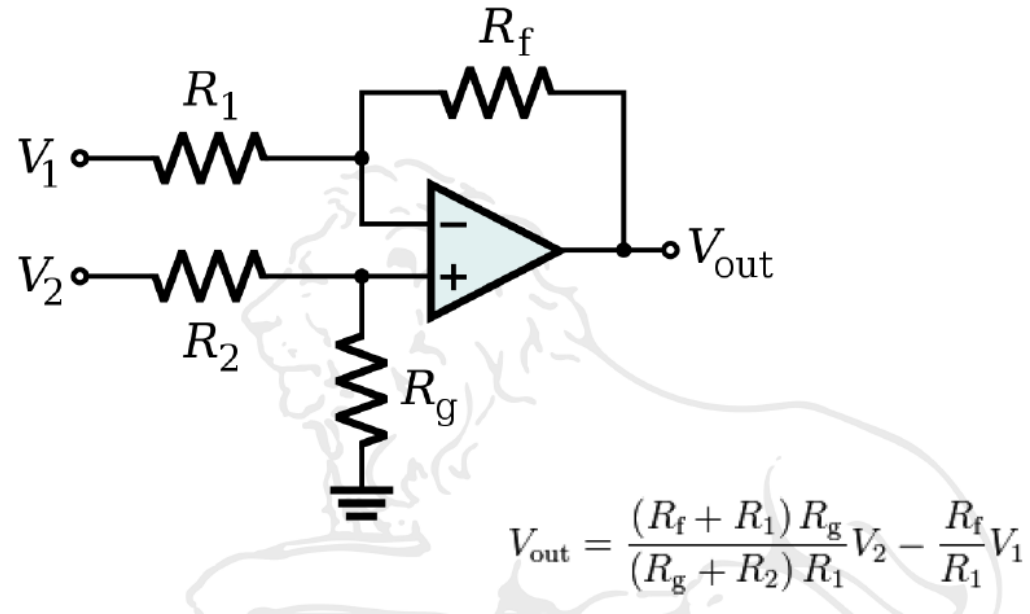


---

If  $R_1 = R_2$  and  $R_f = R_g$ : 
$$V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$

# Op-Amp usages

## Buffer/Voltage follower

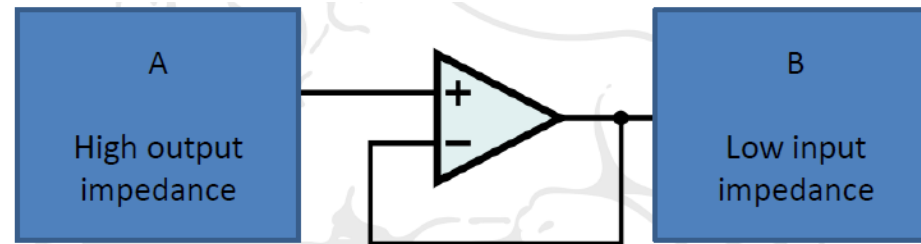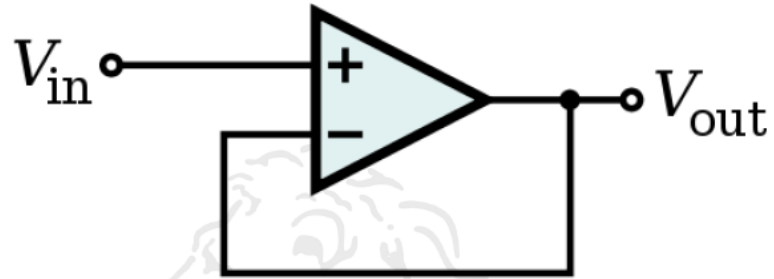



# Question

